


1. Implement $Y(A, B, C, D) = \sum m(0, 1, 6, 7, 8, 9, 10, 11, 12, 14)$ using 16-to-1 multiplexers and 8-to-1 multiplexers.

→ 16 x 1 Mux :- $2^4 = 16 \therefore 4$ select lines

$A = S_3, B = S_2, C = S_1, D = S_0$

N.K.T,

	A	B	C	D	Y
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	1
4	0	0	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

 


8x1 MUX :- $2^3 = 8 \therefore 3$ select lines

A, B, C \rightarrow Select lines

D \rightarrow Input

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
\overline{D}	0	2	4	6	8	10	12	14
D	1	3	5	7	9	11	13	15
	1	0	0	1	1	1	\overline{D}	\overline{D}

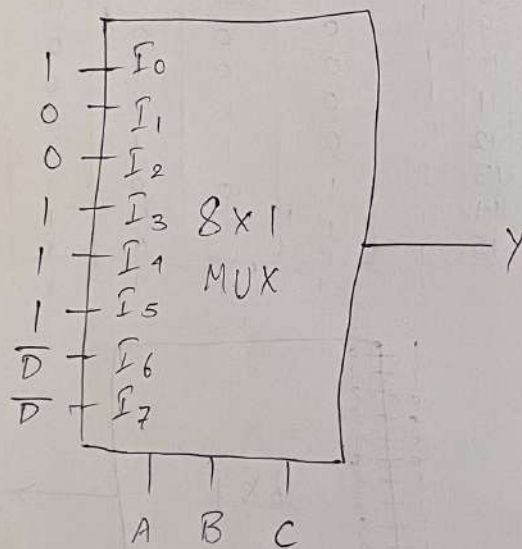

2. Explain different modelling styles used to write the code in VERILOG with an example.

→ 1. Behavioral modelling :- Describes what the circuit does, not how it is built. The logic is described using an if-else statement inside an always block & it is suitable for algorithmic & control logics.

Ex, module and-gate-behavioral(
input A,B;
output reg Y;);
always @(*) begin
if (A & B)
Y = 1'b1;
else
Y = 1'b0;
end
endmodule

2. Dataflow Modelling :- Describes how data flows from inputs to outputs. The output is continuously assigned the results of A & B and suitable for combinational logic.

Ex, module and-gate-dataflow(
input A,B;
output Y;);
assign Y = A & B;
endmodule

3. Structural Modelling :- Describes the circuit as an interconnection of components using gate-level modules like AND gate as a primitive gate.

Ex, module and-gate-structural(
input A, B;
output Y;)
and G1 (Y, A, B);
endmodule

3. Find the complement & simplify the Boolean function and also write logic circuit $F = A'B'C' + A'BC$.

→ Given Boolean function,

$$F = A'B'C' + A'BC$$

$$\Rightarrow F = A'(B'C' + BC)$$

Complement :- $F' = [A'(B'C' + BC)]'$

Apply De Morgan's theorem

$$F' = A + (B'C' + BC)'$$

$$\Rightarrow (B'C' + BC)' = (B'C')'(BC)' = (B+C)(B'+C')$$

$$\therefore F' = A + (B+C)(B'+C')$$

$$\text{But, } (B+C)(B'+C') = BC' + B'C$$


$$\text{Hence, } F' = A + B'C + BC'$$

Simplification:- The expression is XNOR of B & C


$$B'C' + BC = (B \odot C)$$

$$\therefore F = A'(B \odot C) \Rightarrow F = A'(B'C' + BC)$$

Logic Circuit:-

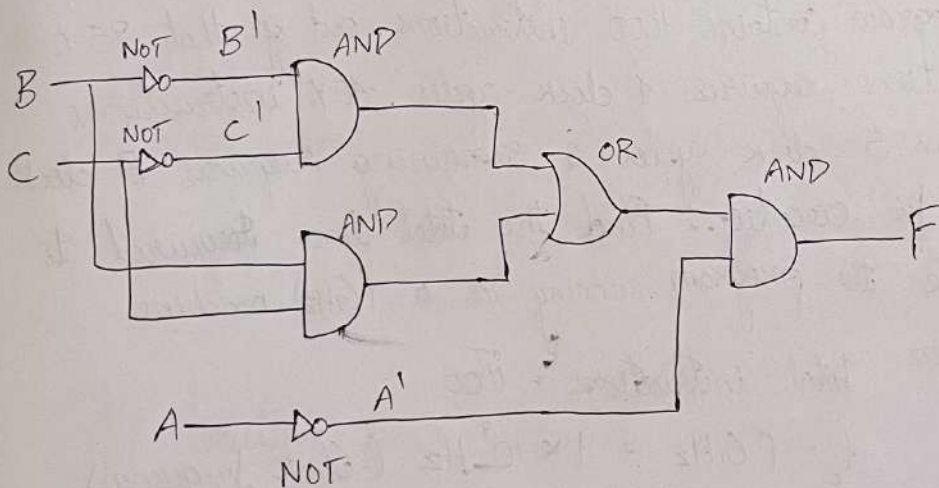

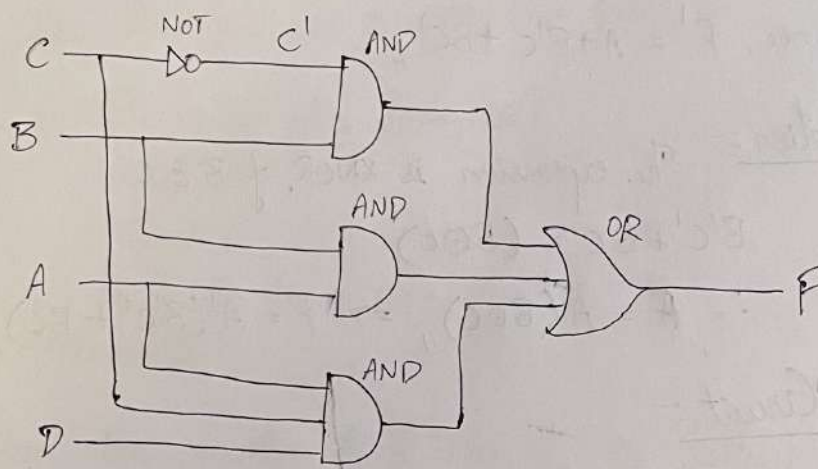4. Draw a 2-level logic diagram to implement the boolean function $F = BC' + AB + ACD$.



5. A program contains 1000 instructions. out of that 25% instructions requires 1 clock cycles, 40% instructions requires 5 clock cycles & remaining requires 3 clock cycles for execution. Find the total time required to execute the program running in a 1GHz machine.

→ Given, Total instructions = 1000

$$f_c = 1 \text{ GHz} = 1 \times 10^9 \text{ Hz (Clock frequency)}$$

$$T_c = \frac{1}{f} = \frac{1}{10^9} = 1 \text{ ns, (Clock Period)}$$

* 25% requires 4 cycles :-

$$0.25 \times 1000 = 250 \text{ instructions}$$

$$250 \times 4 = 1000$$

* 40% requires 5 cycles :-

$$0.40 \times 1000 = 400 \text{ instructions}$$

$$400 \times 5 = 2000$$

* Remaining require 3 cycles :-

$$1000 - (250 + 400) = 350 \text{ instructions}$$

$$350 \times 3 = 1050$$

$$\text{Total clock cycles} = 1000 + 2000 + 1050 = 4050 \text{ cycles}$$

$$\text{Execution Time} = \text{Total cycles} \times \text{Clock period}$$

$$= 4050 \times 1 \text{ ns}$$

$$= 4050 \text{ ns}$$

$$\text{Total execution time} = 4050 \text{ ns} = 4.05 \mu\text{s}$$

6. Design a car safety alarm circuit diagram. The system consider 4 inputs :- Door (D), Key (K), Seat pressure (P) and seat belt (B). The inputs is considered HIGH (1) if the door is closed, the key is in, the driver seat is on the seat, or the seat belt is fastened. The alarm (A) should sound with 2 conditions as stated below :- The door is not closed, & the key is in. The door is closed, the key is in the driver's seat & the seat belt is not closed.

(a) Construct a truth table for the system based on input arrangement D, K, P, B with A as an output.

→ Given, D = Door closed, K = Key inserted, P = Driver seat
B = Seat belt fastened, A = Alarm (output)

∴ Truth Table :-

D	K	P	B	A
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

$$A = \sum m(4, 5, 6, 7, 14)$$

(b) Design a Karnaugh map to verify the simplified expression.

→

	PB	P'B'	PB'	PB	P'B
DK					
D'K'					
	0	1	3	2	
DK'	1	1	1	1	
	4	5	7	6	
DK				1	
	12	13	15	14	
D'K					
	8	9	11	10	


$$A = D'K + DKPB'$$

$$\therefore A = K(D' + DPB')$$

(c) Draw the simplified circuit using NOR gates only.

→ using De Morgan's Theorem,

$$A = [(K') + (D' + DPB')]'$$

 

7. Define decoder. Describe the working principle of a 3:8 decoder. Draw the logic circuit diagram of the 3:8 decoder with enabled inputs. Realize the following boolean expressions using a 3:8 decoder and multi-input OR gates :- $F_1(A, B, C) = \sum m(1, 3, 7)$, $F_2(A, B, C) = \sum m(2, 3, 5)$.


→ A decoder is a combinational logic circuit that converts any n -bit binary inputs into one of 2^n mutually exclusive outputs.

For a given input combination, only one output is active, while all others remain inactive.


Truth Table of 3:8 decoder (with enabled)

E	A	B	C	Y_0	Y_1	Y_2	Y_3	Y_4	Y_5	Y_6	Y_7
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1

Logic diagram:-

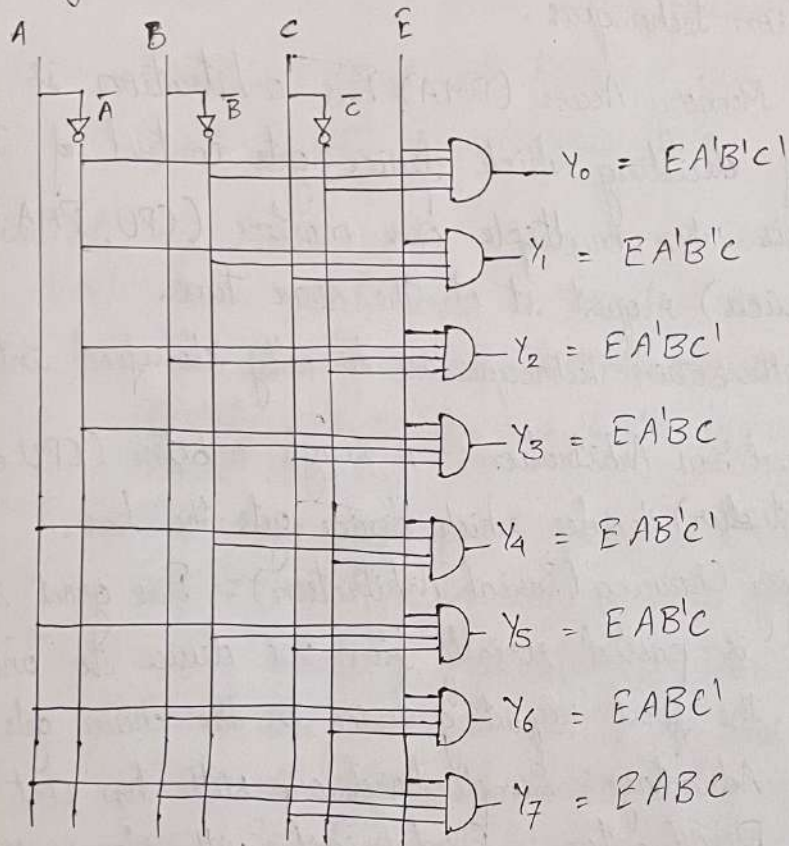

 Realization:- $F_1 = Y_1 + Y_3 + Y_7$, $F_2 = Y_2 + Y_3 + Y_5$ (Given)



8. What is DMA Bus arbitration? Explain different bus arbitration techniques.

→ Direct Memory Access (DMA) Bus arbitration is the process of deciding which device gets control of the system bus when multiple bus masters (CPU, DMA Controller, I/O devices) request it at the same time.

The bus arbitration techniques are broadly classified into:-

* Centralized Bus Arbitration:- A single arbiter (CPU or Bus controller) decides which device gets the bus.

→ Daisy Chaining (Serial Arbitration):- Bus grant signal is passed serially from one device to another & the first requesting device in the chain gets priority.
Advantage:- Simple hardware with low cost.
Disadvantage:- Fixed priority with slower response for low priority devices.

→ Parallel Priority Arbitration:- Each device has a separate request line & arbiter selects the highest priority request.

Pros:- Fast arbitration with flexible priority assignment.

Cons:- More hardware & complex design.

→ Rotating Priority (Round Robin) :- Priority rotates after each bus grant which prevents starvation.

Pros:- Fair access with balanced bus usage.

Cons:- Slightly more complex logic.

er, * Distributed Bus Arbitration :- There is no central arbiter. Each device participates in arbitration.

→ Self-Selection Arbitration :- All devices place their priority code on the bus & the highest priority device wins.

Pros:- No single point of failure (Fast Arbitration).

Cons:- More logic in each device & higher cost.

→ Collision-Detection Arbitration :- Devices start transmitting simultaneously so that the collision is detected & devices retry after delay.

Pros:- Simple concept & no arbiter required.

Cons:- Collisions waste time & not ideal for DMA. (real-time).

9. Explain, with an example, the different types of hazards that occur during pipelining.

→ There are 3 types of hazards:-

* Structural Hazards :- This occurs when 2 or more instructions require the same hardware resource at the same time, but the hardware cannot support all requests simultaneously.

Ex, I1: LOAD R1, 0(R2)
I2: ADD R3, R1, R4

* Data Hazards :- This occurs when an instruction depends on the result of a previous instruction that has not yet completed execution.

Ex, (a) RAW (Read after write) :- I1: ADD R1, R2, R3
I2: SUB R4, R1, R5

(b) WAR (Write after read) :- I1: SUB R3, R1, R2

(c) NAW (Write after write) :- I1: ADD R1, R4, R5
I2: MUL R1, R2, R3
I2: ADD R1, R4, R5

* Control Hazards :- This occurs due to branch or jump instructions, where the next instruction depends on the outcome of a branch.


Ex, I1: BEQ R1, R2, LABEL
I2: ADD R3, R4, R5

10. Explain the basic operation concepts of the computer with a neat diagram.

→ A Computer performs its operations based on the stored-program concepts, where both data & instructions are stored in memory and the processor executes instructions one by one.

Main functional units of a Computer :-

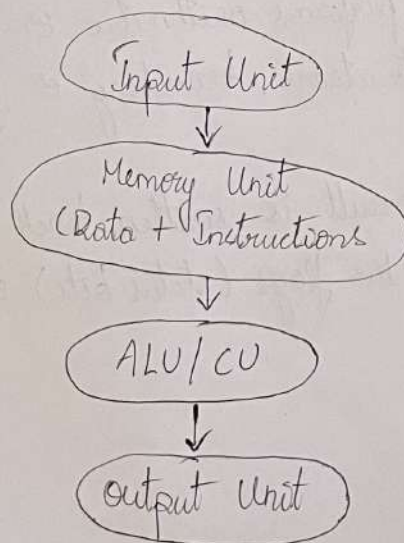- * Input Unit
- * Memory Unit
- * Central Processing unit (CPU) :- Arithmetic Logic Unit (ALU)
Control Unit (CU)
Registers.
- * output Unit
- * System Buses (Data, Address).



There are 5 basic operations :- (Instruction Execution Cycle)

- * **Instruction Fetch** :- The Program Counter (PC) holds the address of the next instruction. This address is sent to memory where the instruction is fetched & stored in the Instruction Register (IR). PC is then incremented to the next instruction.
- * **Instruction Decode** :- The Control Unit (CU) decodes the instructions in IR. It identifies the operation to be performed, operands required & addressing mode.
- * **Operand Fetch** :- If required, operands are fetched from registers, memory & input devices.
- * **Execute** :- The ALU performs arithmetic or logical operations. For control instructions, branching or jumping is performed.
- * **Write Back** :- The result is written back to register & memory where the flags (status bits) are updated.